

## POWER ELECTRONICS LAB QUESTION

TIME:1 HOUR

1. Simulation of Three phase Bridge Voltage Source Inverter ( $120^\circ$  mode) with (i) R, (ii) R-L load by using MATLAB-Simulink (phase and line voltage). [BT17EE011](#)
2. Simulate of single phase voltage controller for R, R-L, and R-L-E by using MATLAB-Simulink. (\*firing angle= $60^\circ$  and  $150^\circ$ ) [BT17EE017](#)
3. Simulate step down chopper for R, R-L, and R-L-E load by using MATLAB-Simulink. (Duty cycle=30% and 50%) [BT18EE001](#)
4. Simulation of Three phase Bridge Voltage Source Inverter ( $180^\circ$  mode) with (i) R, (ii) R-L load by using MATLAB-Simulink (phase and line voltage) [BT18EE003](#)
5. Simulate V-I characteristics of BJT and MOSFET. [BT18EE004](#)
6. Simulate of single phase full-wave controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $30^\circ$  and  $120^\circ$ ) [BT18EE005](#)
7. Simulate of three phase full-wave controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $60^\circ$  and  $150^\circ$ ) [BT18EE006](#)
8. Simulate of single-phase half controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $30^\circ$  and  $150^\circ$ ) [BT18EE007](#)
9. Simulate step up chopper for R, R-L, and R-L-E load by using MATLAB-Simulink. (Duty cycle=40% and 60%). [BT18EE008](#)
10. Simulation of Three phase Bridge Voltage Source Inverter ( $180^\circ$  mode) with (i) R, (ii) R-L load by using MATLAB-Simulink (phase and line voltage) [BT18EE009](#)
11. Simulate of three phase uncontrolled rectifier with R, R-L ad R-L-E load by using MATLAB-Simulink. [BT18EE010](#)
12. Simulate of single-phase half-wave controlled rectifier with R, R-L ad R-L-E load use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $30^\circ$  and  $150^\circ$ ) [BT18EE011](#)
13. Simulate three phase full-wave uncontrolled rectifier in MATLAB Simulink with R, R-L and RLE load. [BT18EE012](#)
14. Simulate of single-phase half-controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $60^\circ$  and  $120^\circ$ ) [BT18EE014](#)
15. Simulate V-I characteristics of MOSFET and SCR. [BT18EE015](#)
16. Simulate of single phase half controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $30^\circ$  and  $150^\circ$ ) [BT18EE016](#)
17. Simulate of single phase full-wave controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $45^\circ$  and  $150^\circ$ ) [BT18EE017](#)
18. Simulate of three phase full-wave controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $30^\circ$  and  $120^\circ$ ) [BT18EE018](#)
19. Simulate V-I characteristics of BJT and SCR. [BT18EE019](#)
20. Simulate of three phase full-wave controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $45^\circ$  and  $120^\circ$ ) [BT18EE020](#)
21. Simulate step down chopper for R, R-L, and R-L-E load by using MATLAB-Simulink. (Duty cycle=40% and 60%) [BT18EE021](#)
22. Simulation of Three phase Bridge Voltage Source Inverter ( $180^\circ$  mode) with (i) R, (ii) R-L load by using MATLAB-Simulink (phase and line voltage) [BT18EE022](#)

23. Simulate V-I characteristics of BJT and MOSFET. [BT18EE023](#)
24. Simulate of three phase full-wave controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $45^{\circ}$  and  $120^{\circ}$ ) [BT18EE024](#)
25. Simulate of three phase uncontrolled rectifier with R, R-L and R-L-E load by using MATLAB-Simulink. [BT18EE025](#)
26. Simulation of Three phase Bridge Voltage Source Inverter ( $180^{\circ}$  mode) with (i) R, (ii) R-L load by using MATLAB-Simulink (phase and line voltage) [BT18EE026](#)
27. Simulate of three phase full-wave controlled rectifier for R, R-L, and R-L-E and also use freewheeling diode by using MATLAB-Simulink. (\*firing angle= $45^{\circ}$  and  $120^{\circ}$ ) [BT18EE027](#)